

DDCO Mini Project ISA Submission

Project Title: 4-bit Up Counter, Down Counter


Section : E

Batch Details


Student Name	SRN
Nemalli Vishnu Vardhan Reddy	PES1UG19CS295
Nerella Venkata Tarunika	PES1UG19CS296
Nihal Ramaswamy	PES1UG19CS297
Nihal Shetty	PES1UG19CS298

Circuit Diagram:

1. Up Counter

 

2. Down Counter

 

Implementation (Code):

//Implementation file

```
module and2 (input wire input_wire0, input_wire1, output wire output_wire);
```

```
    assign output_wire = input_wire0 & input_wire1;
```

```
endmodule
```

```
module or2 (input wire input_wire0, input_wire1, output wire output_wire);
```

```
    assign output_wire = input_wire0 | input_wire1;
```

```
endmodule
```

```
//This is the module for the T flip flop
```

```
module toggle_flip_flop (input wire clock_signal,reset_wire,toggle_wire, output  
data_wire);
```

```
    reg data_wire;
```

```
    always @ (posedge clock_signal)
```

```
    begin
```

```
        if(reset_wire)
```

```
            data_wire=4'b0000;
```

```
        else
```

```
            if(toggle_wire) data_wire=~data_wire;
```

```
            else data_wire=data_wire;
```

end

endmodule

//This module is for the down counter

module down_counter (input wire clock_signal, reset_signal, output
wire[3:0]q);

wire [5:0]a;

wire [2:0]or_out;

toggle_flip_flop t1 (clock_signal, reset_signal, 1'b1, q[0]);

and2 and2_1 (q[0], 1'b0, a[0]);

and2 and2_2 (~q[0], 1'b1, a[1]);

or2 or2_1 (a[0], a[1], or_out[0]);

toggle_flip_flop t2 (clock_signal, reset_signal, or_out[0], q[1]);

and2 and2_3 (q[1], a[0], a[2]);

and2 and2_4 (~q[1], a[1], a[3]);

or2 or2_2 (a[2], a[3], or_out[1]);

toggle_flip_flop t3 (clock_signal, reset_signal, or_out[1], q[2]);

and2 and2_5 (q[2], a[2], a[4]);

and2 and2_6 (~q[2], a[3], a[5]);

or2 or2_3 (a[4], a[5], or_out[2]);

```
toggle_flip_flop t4 ( clock_signal, reset_signal, or_out[2], q[3]);
```

```
endmodule
```

```
//This module is for the up counter
```

```
module up_counter (input wire clock_signal, reset_signal, output wire[3:0]q);
```

```
    wire [5:0]a;
```

```
    wire [2:0]or_out;
```

```
    toggle_flip_flop t1 ( clock_signal, reset_signal, 1'b1, q[0]);
```

```
    and2 and2_1 (q[0], 1'b1, a[0]);
```

```
    and2 and2_2 (~q[0], 1'b0, a[1]);
```

```
    or2 or2_1 (a[0], a[1], or_out[0]);
```

```
    toggle_flip_flop t2 ( clock_signal, reset_signal, or_out[0], q[1]);
```

```
    and2 and2_3 (q[1], a[0], a[2]);
```

```
    and2 and2_4 (~q[1], a[1], a[3]);
```

```
    or2 or2_2 (a[2], a[3], or_out[1]);
```

```
    toggle_flip_flop t3 ( clock_signal, reset_signal, or_out[1], q[2]);
```

```
    and2 and2_5 (q[2], a[2], a[4]);
```

```
    and2 and2_6 (~q[2], a[3], a[5]);
```

```
    or2 or2_3 (a[4], a[5], or_out[2]);
```

```
toggle_flip_flop t4 ( clock_signal, reset_signal, or_out[2], q[3]);
```

```
endmodule
```

```
//Testbench
```

```
module counter_tb();
```

```
reg clock,reset;
```

```
wire [3:0]q_up,q_down;
```

```
//This calls up counter
```

```
up_counter uc(clock,reset,q_up);
```

```
//This calls down counter
```

```
down_counter dc(clock,reset,q_down);
```

```
initial begin
```

```
    $dumpfile("counter4_tb.vcd");
```

```
    $dumpvars(0,counter_tb);
```

```
end
```

```
initial
```

```
begin
```

```
clock=0; repeat(70) #10 clock=~clock;
```

```
end
```

//This is where the reset wire becomes 1 and 0 accordingly

initial

begin

reset=1'b1;

#30

reset=1'b0;

#160

reset=1'b1;

#20

reset=1'b0;

end

endmodule

//Link to project: <https://github.com/nihal-ramaswamy/DDCO-project>

Output:

